

Science Skills Year 8 booklet: 3

Ohm's Law

Task 1 deadline (self-assessed):

Task 2 deadline (peer-assessed):

Task 3 deadline (teacher-assessed):

The tasks in this booklet relate to the investigation below. Read the following information before attempting any of the tasks.

Method:

Set up a circuit which contains a fixed resistor, ammeter and a voltmeter
Starting at 0V, take the measurement of the current. Increase the voltage by 0.5V until you reach 5V, measuring the current at each step.

Results:

Voltage Level (V)	Resistance (Ohms)	Current (A)
0.0	10	0
0.5	10	0.05
1.0	10	0.1
1.5	10	0.15
2.0	10	0.2
2.5	10	0.25
3.0	10	0.3
3.5	10	0.35
4.0	10	0.4
4.5	10	0.45
5.0	10	0.5

Task 1

Everyone to do- Match the key terms to the definitions:

Voltage	A flow of electrons.
Current	Also known as potential difference. The difference in energy between two points on a circuit.
Resistance	Something which opposes (goes against) the flow of electrons in a circuit.
Voltmeter	A device which measures current.
Ammeter	A device which measures voltage.

Green: you will be tested on the spelling of the five key terms

Amber: you will be tested on the spelling and the definition of the key terms

Red: you will be tested on the spelling and definition of the key terms. You will also need to put each into a sentence

Killer: you will be asked for synonyms for the key terms (if there are any!)

Task 2

Green:

On paper, draw a circuit diagram for the one which was set up in this investigation. Remember to use the correct circuit symbols.

Peer assessment:

STAR:

STAR:

WISH:

Amber:

The current flowing **through** a resistor at a constant temperature is directly proportional to the voltage **across** the resistor. So, if you double the voltage, the current also doubles. This is called Ohm's Law.

Explain whether or not the data in the table supports this statement.

Peer assessment:

STAR:

STAR:

WISH:

Red:

The equation for calculating resistance is:

potential difference (volt, V) = current (ampere, A) × resistance (ohm, Ω)

Pick 4 results from the table and calculate the voltage to check the results.

Explain whether or not the data in the table supports the relationship between current through a resistor and voltage being directly proportional.

Peer assessment:

STAR:

STAR:

WISH:

Task 3:

Green: On a piece of graph paper, plot the results of this investigation. You should put voltage on the x axis (across the bottom) and current on the y axis (up the side). Use a line graph and your scale should be one square for 0.5V and one square for 0.5A.

Amber: On a piece of graph paper, plot a graph of the results. Think carefully about your scale and remember that you should put voltage on the x axis (across the bottom) and current on the y axis (up the side).

Red: On a piece of graph paper, plot a graph of the results. You will not need to plot all pieces of information in the table.

Teacher assessment:

A2L = 1	Work is thorough, you have picked challenging tasks and have shown effort and understanding.
A2L = 2	Work has detail in most places, you have picked relevant tasks and have shown effort.
A2L = 3	Work lacks detail, there are some errors and shows some lack of preparation/understanding.
A2L = 4	Work is incomplete, there are errors throughout and a clear lack of preparation/understanding.

Teacher comment: